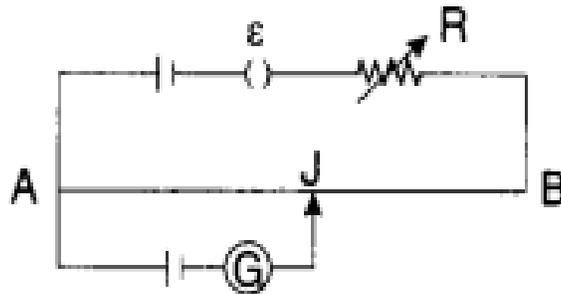


National Institute of Open Schooling
Senior Secondary
Lesson 17-ELECTRIC CURRENT
WORKSHEET – 17


Q1. A cell having an emf E and internal resistance r is connected across a variable external resistance R . As the resistance R is increased, plot the graph of potential difference V across R .

Q2. In a Wheatstone bridge if the battery and galvanometer are interchanged then comment upon the deflection in galvanometer.



Q3. A steel wire is stretched to make it 0.2% longer. What is the percentage change in its resistance and resistivity?

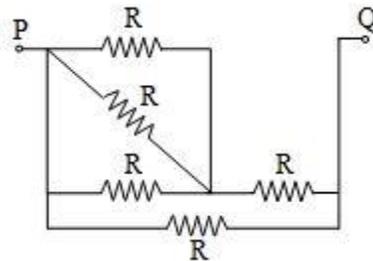
Q4. The equivalent resistance between the terminal point P and Q is 4Ω in the given circuit. Find out the resistance of R in ohms.



Q5. Two conducting wires P and Q are having same diameter but made up of different materials. Both the wires are joined in series across a battery. If the number density of electrons in P is 3 times than in Q , find the ratio of drift velocity of electrons in the two wires.

Q6. Two conducting wires X and Y of same diameter but different materials are joined in series to form a battery. If the number density of electrons in X is twice that in Y , find the ratio of drift velocity of electrons in the two wires. Explain if they are connected in parallel?

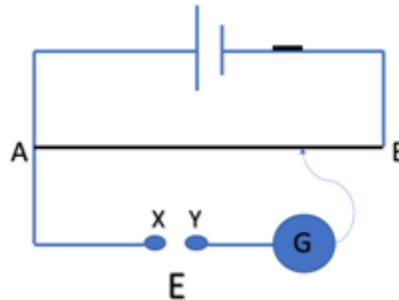
- Q6.** For the potentiometer circuit shown in the given figure point X and Y represent the two terminals of a cell of an unknown e.m.f. E. A student observed that when the jockey is moved from end A to end B of the potentiometer wire, the deflection in the galvanometer remains in the same direction.



- a) What are two possible faults in the circuit that could result in this observation?
- b) If the galvanometer deflection at the end B is
 - i) More than at end A
 - ii) Less than at end A,

Which of the two faults, listed above, would be there in the circuit? Give reasons in support of your answer in each case.

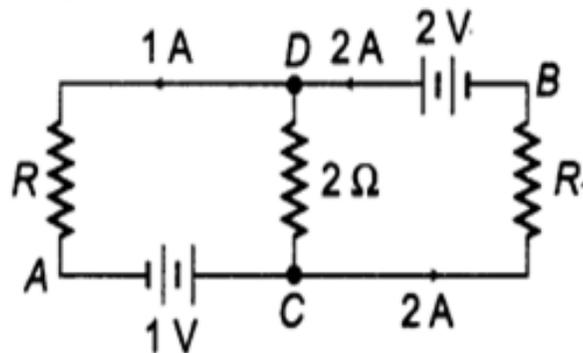- Q8.** In the given circuit, assuming point A to be at zero potential, use Kirchoff's rules to determine the potential at point B



- Q9.** Two tungsten filaments with resistance R_1 and R_2 respectively are connected first in series and then in parallel in a lighting circuit of negligible internal resistance. If $R_1 \gg R_2$ answer the following questions –
- a) Which lamp will glow more brightly when they are connected in series?
 - b) If the lamp of resistance R_2 now burns out and the lamp R_1 alone is plugged in; will net illumination increase or decrease?
 - c) Which lamp will glow more brightly when they are connected in parallel?
 - d) If the lamp of resistance R_1 now burns out, how will the net illumination produced change?
- Q10.** At the temperature 0°C , the electric resistance of conductor B is n times that of conductor A. Their temperature coefficients of resistance are equal to α_2 and α_1 respectively. Find the resistance and temperature coefficients of a resistance of a circuit segment consisting of these two conductors when they are connected in series.